 


Digital Systems

Assignment – 2

Q-1 Design a combinational circuit with three inputs, x , y , z , and three outputs, A , B , C . When the binary input is 4, 5, 6, or 7, the binary output is 2 less than the binary input. When the binary input is 0, 1, 2, or 3, the output is 4 more than the binary input. [3 M]

Q-2 For the S-R latch, assume each NAND gate has a delay of 1 nsec. The inputs to the S-R latch are applied as follows. At every 1 nsec, the value at S is given by 0, 0, 0, 0, 0, 1, 1, 1, 1, 1, 1, 1, 1, 1. At every 1 nsec, the value at R is given by 1, 1, 1, 1, 1, 1, 1, 1, 1, 0, 1, 1, 1, 1. Find out the waveform at the outputs, Q , \bar{Q} as functions of time. What is the “hold time” of this latch? (Here “hold time” is the minimum pulse-width at the input for a reasonable output.) [1M]




Q-3 Design and draw the optimal logic circuit for the 4-bit synchronous counter to count the prime numbers using JK flipflops with a negative edge trigger clock. [2.0 M]


Q-4 Specify the truth table with 4 bits for a Fibonacci number recognizer using Read-Only Memory (ROM). Derive the Boolean function and draw the optimal design circuit for the Fibonacci numbers recognizer using ROM. [3.0 M]

Q-5 [1 M]

 Consider the following circuit with initial state $Q_0 = Q_1 = 0$. The D flip-flops are positive edged triggered and have set up times 20 ns and hold times 0.




 Consider the following timing diagrams of X and C ; the clock period of $C \geq 40$ ns. Which one is the correct plot of y ?



- a)
- b)
- c)
- d)

Q-6 [1M]

 


The above synchronous sequential circuit built using JK flip-flops is initialized with $Q_2Q_1Q_0 = 000$. The state sequence for this circuit for the next 3 clock cycles is

 - a) 001, 010, 011 c) 111, 110, 101
b) 100, 110, 111 d) 100, 011, 001

Q-7 [1M]

For a state machine with the following state diagram the expression for the next state S^+ in terms of the current state S and the input variables x and y is



- a) $S^+ = S'.y' + S.x$
- b) $S^+ = S.x.y' + S'.y.x'$
- c) $S^+ = x.y'$
- d) $S^+ = S'.y + S.x'$


Hint: Explore state machines or state diagrams

Q-8 [2M]

The Control signal functions of a 4-bit binary counter are given below (where x is don't care):

Clear	Clock	Load	Count	Function
1	x	x	x	Clear to 0
0	x	0	0	No change
0	↑	1	x	Load input
0	↑	0	1	Count next

The counter is connected as follows

 


Assume that the counter and gate delays are negligible. If the counter starts at 0, then it cycles through the following sequence

 - a) 0, 3, 4
- b) 0, 3, 4, 5
- c) 0, 1, 2, 3, 4, 5
- d) 0, 1, 2, 3, 4

Q-9 [1M]

Consider the following state diagram and its realization by a JK flip flop.




The combinational circuit generates J and K in terms of x , y and Q . The Boolean expressions for j and K are:

- a) $\overline{x \oplus y}$ and $\overline{x \oplus y}$
- b) $\overline{x \oplus y}$ and $x \oplus y$
- c) $x \oplus y$ and $\overline{x \oplus y}$
- d) $x \oplus y$ and $x \oplus y$

Hint: Explore state machines

Q-10

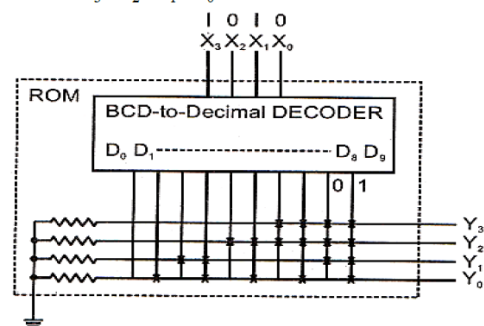If the input X_3, X_2, X_1, X_0 to the ROM in the figure are 8 4 2 1 BCD numbers, then the outputs Y_3, Y_2, Y_1, Y_0 are



- a) gray code numbers
- b) 2 4 2 1 BCD numbers
- c) excess-3 code numbers
- d) none of the above